

Lab Report: Experiment 2

EE24BTECH11003 : Akshara Sarma Chennubhatla
EE24BTECH11005 : Arjun Pavanje

January 29, 2025

Experiment:

Connecting an RC Circuit
giving Square Wave Input
plotting Steady and Transient state
on an Oscilloscope
for 3 cases



भारतीय प्रौद्योगिकी संस्थान हैदराबाद
Indian Institute of Technology Hyderabad

Bachelor of Technology

Department of Electrical Engineering

Objective

To analyze the transient and steady-state responses of an RC circuit to a square wave input ($0 - 5V$) in three cases:

1. $RC \ll T$

2. $RC = T$

3. $RC \gg T$

where T is the time period of the input square wave.

Equipment Used

- Function generator
- Resistor R
- Capacitor C
- Oscilloscope
- Wires

Theory

Procedure

Connecting Circuit

Circuit should be of the below form,


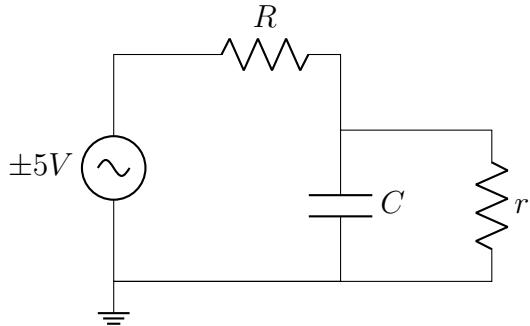


Figure 1: RC Circuit


1. Construct the circuit as shown in the above figures.
 - (a) Connect the positive end of the function generator in series with a resistor
 - (b) Connect the capacitor and a small resistance in parallel, connect the combination in series with the rest of the circuit.
2. Set the function generator to output a square wave with $5V$ amplitude (Peak Voltage V , Minimum Voltage $0V$) and a time-period T . Select the type of cycle as N -CYCLES.
3. Connect the second channel of the function generator to the second channel of the oscilloscope. Set the waveform for this as a square wave with the same conditions as in the first channel. This will allow us to compare output voltage across capacitor with input square wave.
4. This configuration enables the generation of a square wave with a pre-defined number of cycles when the trigger button is pressed on the function generator. On the oscilloscope, press the *SINGLE* button. This ensures that the next event captured by the oscilloscope is displayed and then the display pauses automatically.
5. Trigger the burst mode manually on the function generator to generate the single pulse or event.
6. Observe and record the captured waveforms on the oscilloscope.
7. To capture steady state, switch from burst mode to continuous mode and capture steady state.

Results and Verification

Case 1: $RC \ll T$

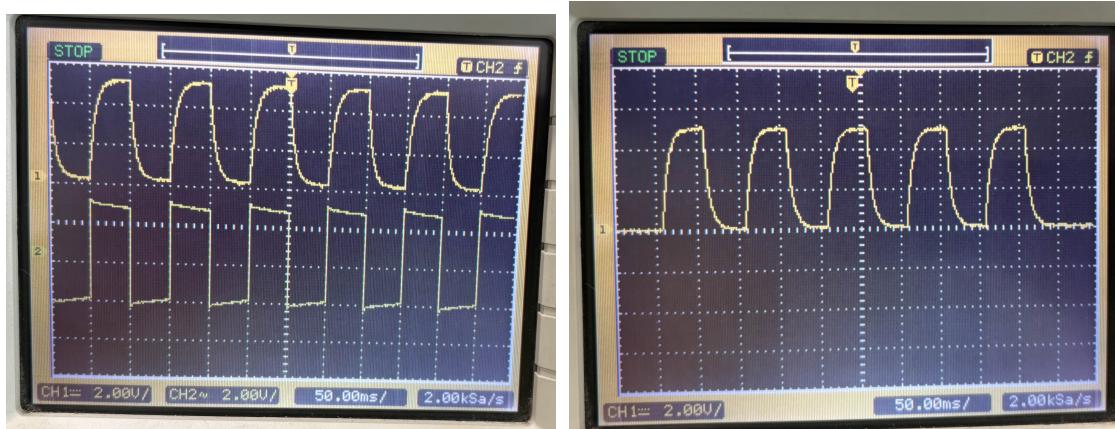


Case 2: $RC = T$

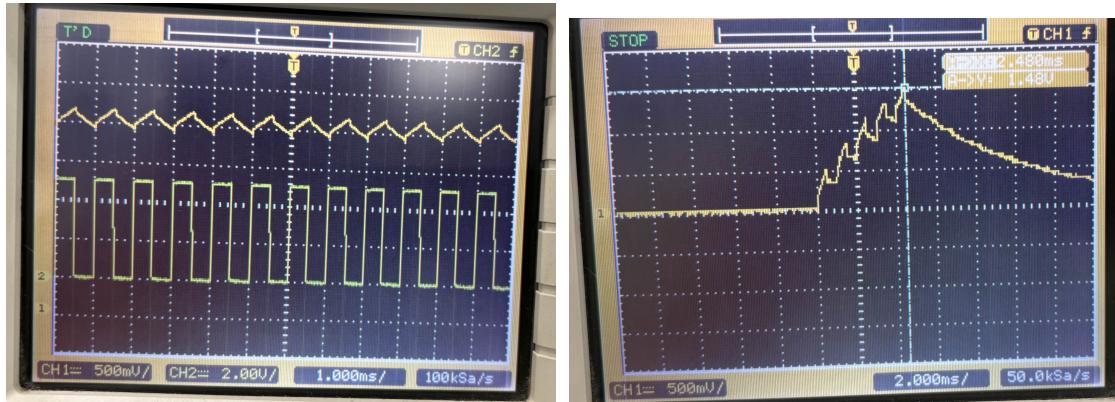

Case 3: $RC \gg T$

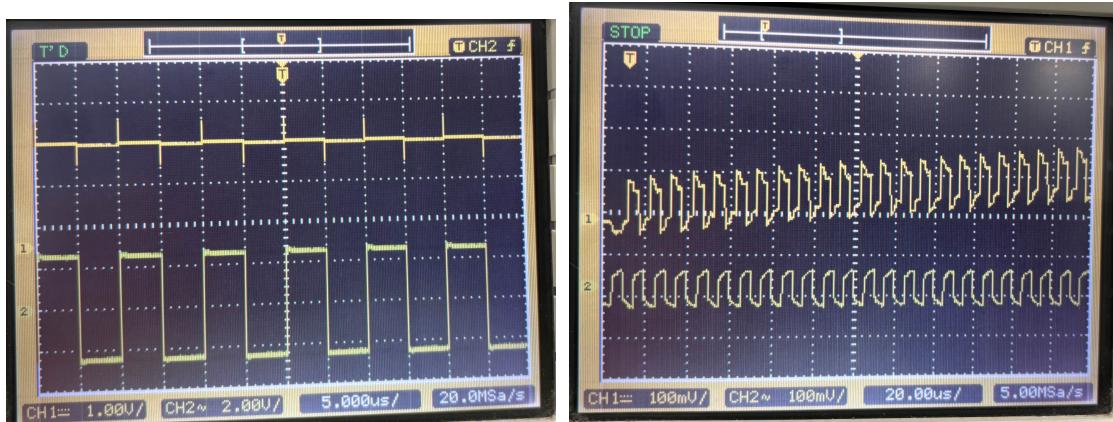Here, we have plotted more than 5 cycles of square wave as it better shows the increasing nature of the potential difference across capacitor.



For an infinite number of cycles of square wave, output comes out to be,



Python code verification of obtained graphs:

https://github.com/ArjunPavanje/EE1200/tree/main/Experiment_2/codes

Conclusion

We have successfully found and verified the effect (output) of a square wave on a series RC circuit.