

Lab Report: Experiment 3

EE24BTECH11003 : Akshara Sarma Chennubhatla

EE24BTECH11005 : Arjun Pavanje

February 25, 2025

Experiment:

Studying the transient
and steady state response
of an RC Circuit
with Square Wave Input



भारतीय प्रौद्योगिकी संस्थान हैदराबाद
Indian Institute of Technology Hyderabad

Bachelor of Technology

Department of Electrical Engineering


1 Introduction

In this experiment, we study and analyze the transient response of an LC circuit, determine the natural frequency (ω_n), and calculate the damping ratio (ξ) using theoretical and experimental methods.

An LC circuit consists of an inductor (L) and a capacitor (C) connected in parallel. When a charged capacitor is connected to an inductor, energy oscillates between the capacitor's electric field and the inductor's magnetic field. The system follows the second-order differential equation.

- Inductance, $2.2mH$
- Capacitance, $450pF$

2 Theory

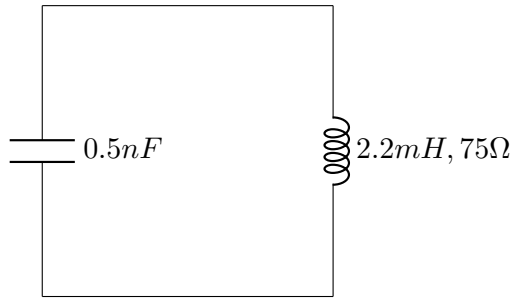

Writing *KVL* equation,

$$L \frac{di}{dt} + iR + \frac{1}{C} \int i dt = 0$$

$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = 0$$

$$\frac{d^2q}{dt^2} + \left(\frac{R}{L} \right) \frac{dq}{dt} + \frac{q}{LC} = 0$$

Let

$$\omega_n = \frac{1}{\sqrt{LC}},$$
$$\xi = \frac{R}{2} \sqrt{\frac{C}{L}}.$$

Substituting these into the equation:

$$\frac{d^2q}{dt^2} + 2\xi\omega_n\frac{dq}{dt} + (\omega_n^2)q = 0$$

Here, $\xi < 1$, so the system is underdamped.

The solution for $q(t) = e^{st}$ will have complex conjugate roots:

$$s = -\xi\omega_n \pm j\omega_d,$$

where $\omega_d = \omega_n\sqrt{1 - \xi^2}$.

Thus, the current $i(t)$ can be written as:

$$q = Ce^{-\xi\omega_n t}e^{j\omega_d t} + C^*e^{-\xi\omega_n t}e^{-j\omega_d t}$$

Expanding this:

$$q = Ae^{-\xi\omega_n t} \cos(\omega_d t + \phi).$$

ϕ, A are constants that can be determined using initial conditions. We know $i\Big|_{t=0} = 0$, and $q\Big|_{t=0} = CV_{DC}$

Substituting $q(0) = CV_{DC}$,

$$CV_{DC} = A \cos(\phi). \tag{1}$$

The current $i(t)$ is given by,

$$i(t) = \frac{dq}{dt},$$

$$i(t) = -Ae^{-\xi\omega_n t}(\xi\omega_n \cos(\omega_d t + \phi) + \omega_d \sin(\omega_d t + \phi)).$$

At $t = 0$,

$$i(0) = -A(\xi\omega_n \cos(\phi) + \omega_d \sin(\phi)).$$

Substituting $\frac{dq}{dt}\Big|_{t=0} = 0$,

$$0 = -A(\xi\omega_n \cos(\phi) + \omega_d \sin(\phi)).$$

Simplifying,

$$0 = \xi\omega_n \cos(\phi) + \omega_d \sin(\phi). \tag{2}$$

From (1), (2) we get,

$$\phi = \tan^{-1} \left(-\frac{\xi \omega_n}{\omega_d} \right)$$
$$A = \frac{CV_{DC}}{\cos(\phi)}$$

We finally get,

$$q(t) = \left(\frac{CV_{DC}}{\sqrt{1 - \xi^2}} \right) e^{-\xi \omega_n t} \cos \left(\omega_d t + \tan^{-1} \left(-\frac{\xi \omega_n}{\omega_d} \right) \right).$$

Where, $\xi = \frac{R}{2} \sqrt{\frac{C}{L}}, \omega_n = \frac{1}{\sqrt{LC}}, \omega_d = \omega_n \sqrt{1 - \xi^2}$

3 Procedure

- First, fully charge the capacitor using a DC voltage source (here, we have used 5V).
- Then carefully disconnect the capacitor from charging and connect it in parallel with an inductor (preferably one of large inductance).
- Measure the voltage across either the inductor or capacitor (we have measured across inductor for convenience) using an oscilloscope.
- Using the oscilloscope, set it in the *single* mode and adjust the trigger level accordingly so that the voltage decay across the inductor (or capacitor) can be observed and captured properly.
- Be careful not to charge the capacitor when it is connected in parallel to the inductor, as the inductor might blow up.

4 Experimental Data

Resistance 25Ω ,


Capacitance $460pF$

Inductance, $2.2mH$


Python code used for verification can be found below,

https://github.com/ArjunPavanje/EE1200/tree/main/Experiment_4/codes

(a) Experimental plot

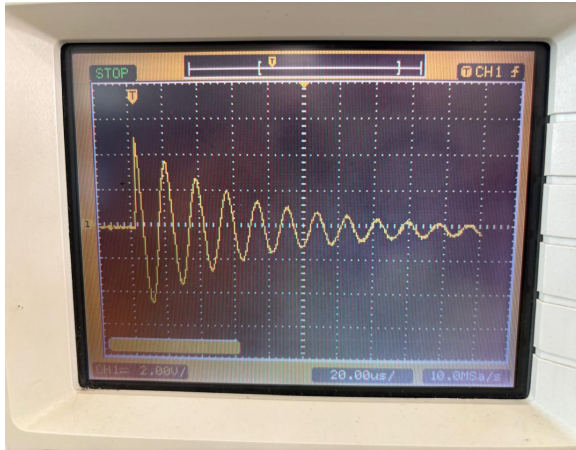

(b) Theoretical plot

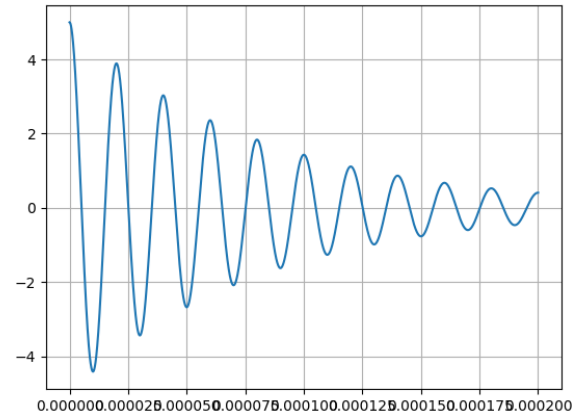

5 Conclusion

In this experiment, we derived the equation for the damped oscillation of a series RLC circuit and verified it experimentally.